
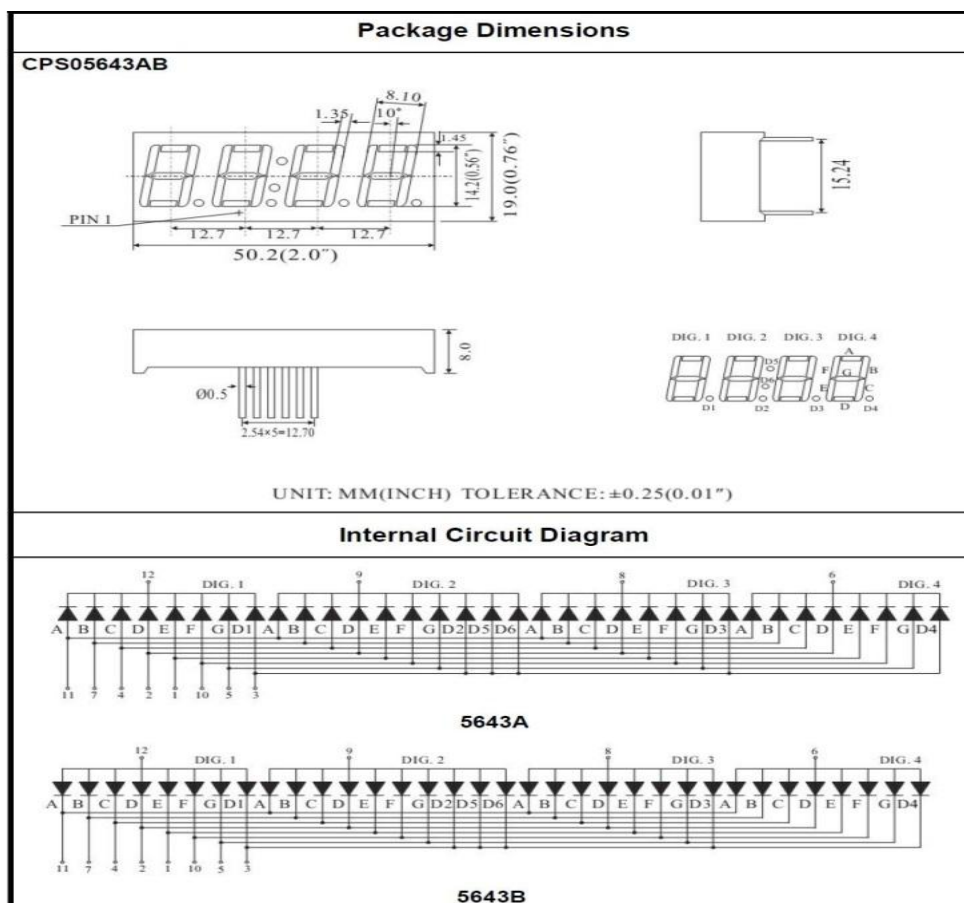


4-Digit 7-Segment Display

Introduction

 We used a 7-segment tube before. When we want to display more than one number, then multidigit tube is required. Here we introduce four digital tube, actually each individual 7-segment tube is almost the same as the tube used above. In this experiment, we will use the Arduino to drive a common anode four digital tube.



Four Digits Displays Series

Four digital tube has 12 pins. The upper left is the biggest number 12 pin. Besides the 8-segment we used to display “adbcdefg”, there are another 4 pins D1, D2, D3, D4 to be used as the “bit” pins. When the “bit” pins of common anode four digital tube is high level, the corresponding tubes light up. The display principle of four digital tube is that constantly scanning D1, D2, D3, D4, and then the corresponding eight-segment tubes will light up in turn. Due to the residual effect of human eye, so it looks like the four digital tube display at the same time.

With the principle introduced above, we now make a simulated countdown time bomb like the movies do. The bomb will exploded in one minute.

Experiment Principle


The most important purpose of this program is how to scan the four digital tube dynamically. In fact, with the single digital tube display experiment before, the display of four digital tube is quite easy. Due to it is attributed to a common anode tube, first of all, we are going to set D1, D2, D3, D4 to low level, all LED turn out, then we output the truth table of “adbcdefg” to the corresponding gpio port, select the corresponding bit pins and scan constantly. How to implement the 1 minute countdown? In the program, we will continuously get the current time through millis () function and determine whether it is greater than 1000ms. If so compared to the time before, the countdown time minus 1, then it is translated into character string that the Nixie tube displays.

Experiment Purpose

The aim is to display “1234” four characters via dynamically scanning 4-Digit 7-Segment Display.

Component List

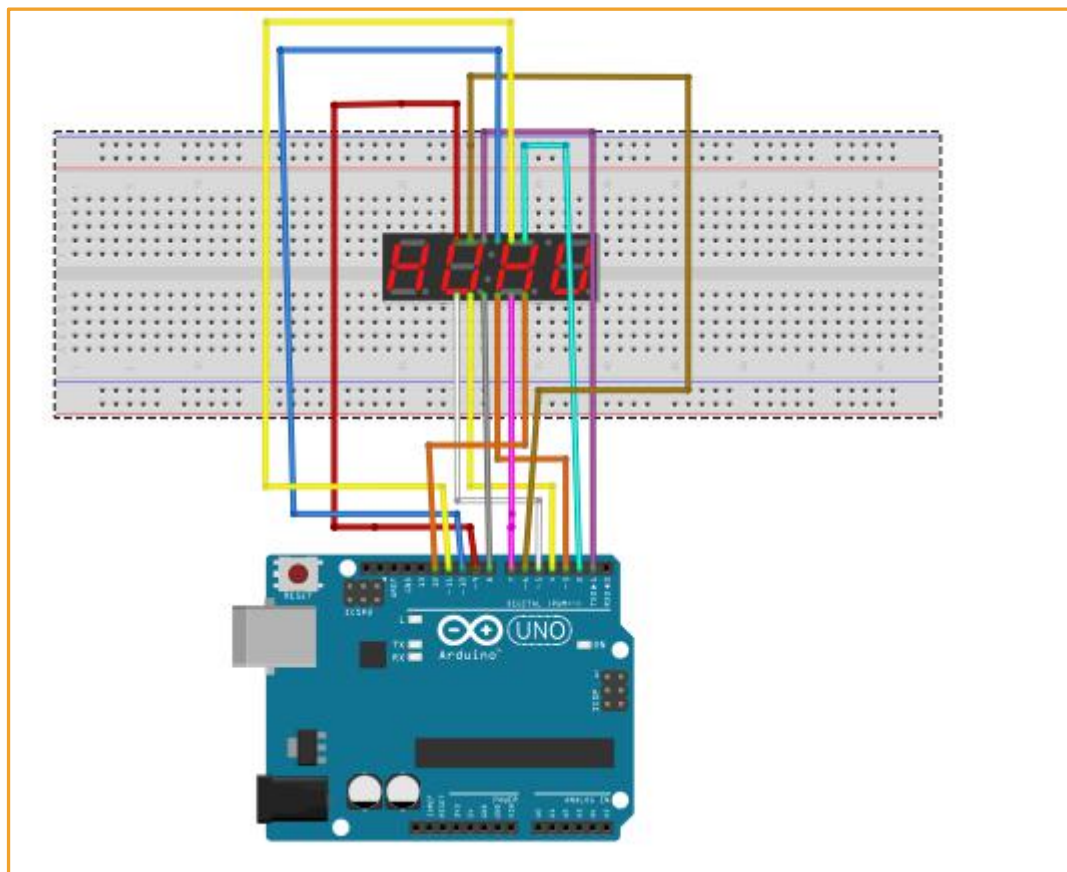- ◆ Keywish Arduino UNO R3 Mainboard
- ◆ Breadboard
- ◆ USB cable
- ◆ 4-Digit 7-Segment Display * 1
- ◆ 1k Resistor * 8
- ◆ 4.7k Resistor * 4
- ◆ Several jumper wires



Code

```
#include "SegmentDisplay.h"


#define LED_A 13      // define Arduino GPIO1 for led a
#define LED_B 2       // define Arduino GPIO2 for led b
#define LED_C 3       // define Arduino GPIO3 for led c
#define LED_D 4       // define Arduino GPIO4 for led d
#define LED_E 5       // define Arduino GPIO5 for led e
#define LED_F 6       // define Arduino GPIO6 for led f
#define LED_G 7       // define Arduino GPIO7 for led g
#define LED_H 8       // define Arduino GPIO8 for led h
#define LED_D1 9
#define LED_D2 10
#define LED_D3 11
#define LED_D4 12
SegmentDisplay _4Bit_7SegmentDisplay(LED_A, LED_B, LED_C, LED_D, LED_E, LED_F, LED_G,
LED_H, LED_D1, LED_D2, LED_D3, LED_D4); //初始化对象，把显示段和片选引脚初始化
int ShowTime = 60, count = 0;
void setup()
{
    Serial.begin(9600);
    _4Bit_7SegmentDisplay.TurnOffAllLed(); //先熄灭所有发光段
}

void loop()
{
    if (count++ > 50 )
    {
        ShowTime-- ;
        count = 0 ;
        Serial.println(ShowTime);
    }
    _4Bit_7SegmentDisplay.DisplayChar((int)ShowTime); //不断刷新要显示的数字注意是 int 型
    delay(5);
    if (ShowTime == 0) {
        _4Bit_7SegmentDisplay.TurnOffAllLed();
        while(1);
    }
}
```

Notice : The 4 numeric digits are converted into the value of AscII by number2dis, say, we are going to convert “1234”, this should be as follows

Loop	numble	bit_base	disp
1	1234	1000	1
2	234	100	2
3	34	10	3
4	4	1	4

Experiment Result

 

Mblock programming program

Mblock writtes 4-Digit 7-Segment Display program as shown in the figure below:

